

Chapter 13 Review, pp. 504–505

8. 1 : 5

Chapter 14 Review, pp. 538–539

3. (a) 0.75 V

(b) 3.0 V

(c) 4.5 V

5. (a) 1 : 20

(b) 5.0 A

6. 8.0 V

7. 16 mA

8. 3.0×10^1 A**Unit 5 Review, pp. 542–545**2. (a) 6.4×10^{-7} C(b) -9.9×10^{-8} C3. (a) 5.0×10^{-9} C(b) -9.9×10^{11} 4. 6.3×10^3 C

7. 120 V

8. (a) 0.86 A

(b) 7.7 W

(c) 2.3×10^2 J

(d) 26 C

(e) 1.6×10^{20}

9. \$15

10. Diagram (a)

(a) $I_1 = I_2 = I_3 = 1.0$ A(b) $V_1 = 2.0$ V; $V_2 = 3.0$ V; $V_3 = 1.0$ V(c) 1.1×10^4 J

Diagram (b)

(a) $I_1 = 4.0$ A; $I_2 = 3.0$ A; $I_3 = 2.0$ A(b) $V_1 = V_2 = V_3 = 12.0$ V(c) 1.9×10^5 J

Diagram (c)

(a) $I_1 = 1.0$ A; $I_2 = I_3 = I_4 = 0.50$ A(b) $V_1 = 7.0$ V; $V_2 = 3.0$ V; $V_3 = 1.0$ V; $V_4 = 2.0$ V(c) 1.8×10^4 J11. (a) 10 Ω (b) 30 Ω

(c) 0.80 A

16. (a) -4.0 V

(b) 2.8 V

(c) 2.0 V

(d) 8.0 V

17. (a) 300 V

(b) 150

18. 100

20. (a) 0.80 A

(b) 0.77 W

(c) 1.9×10^{-6}